
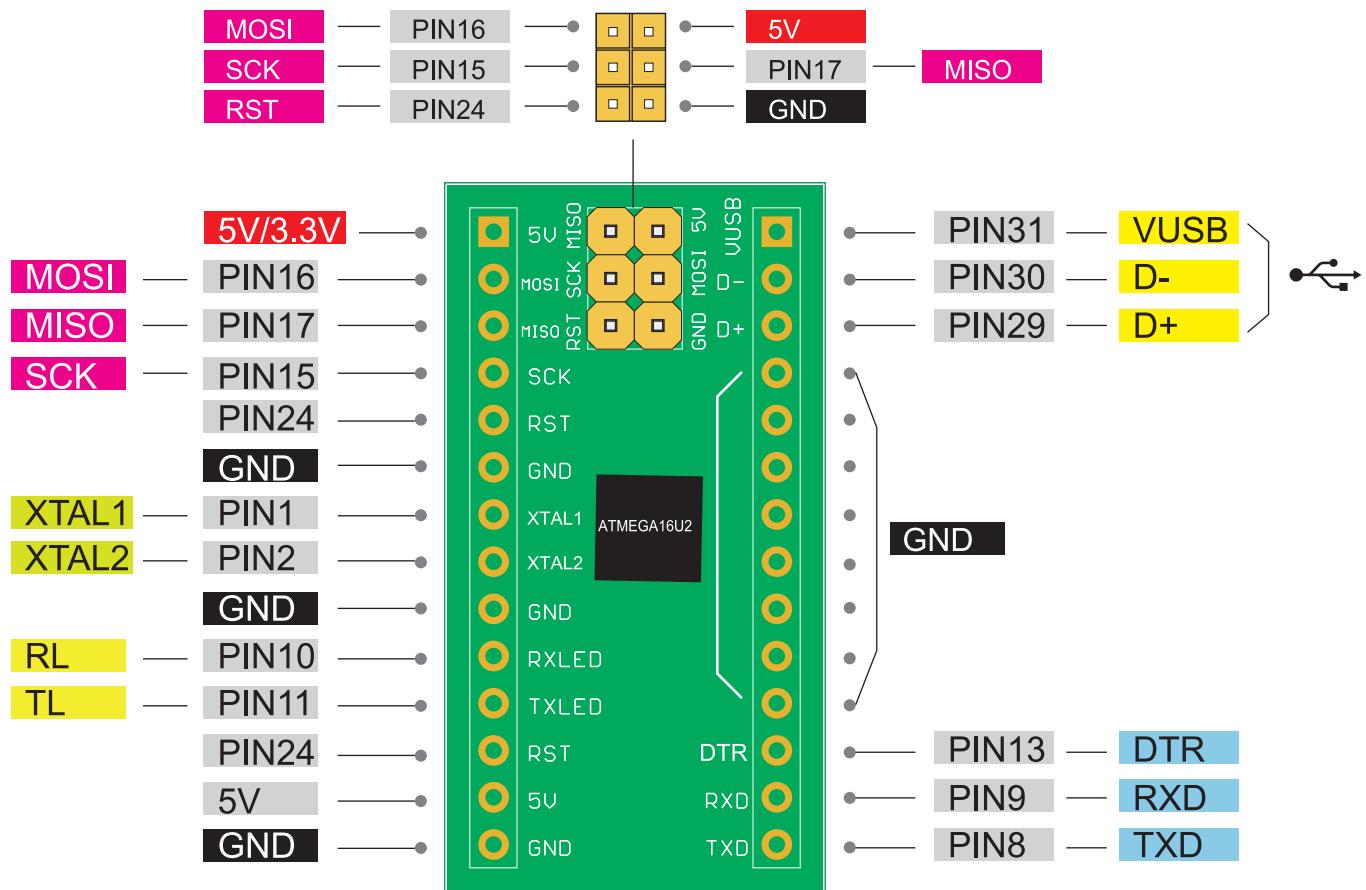



UNO: USB to Serial

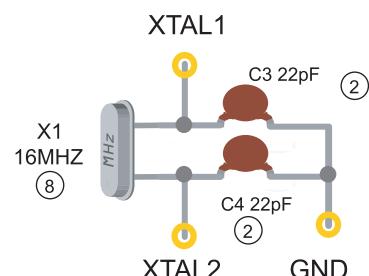

LED: TL: 16U2 is sending data
RL: 16U2 is receiving data




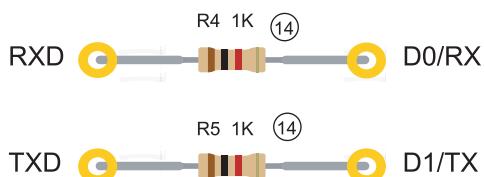Oscillator: This parts must be connected to 16U2 for providing a stable clock signal



Connect to 328p
Bridge between 16U2 & 328P
To flash the MCU with UART,
16u2 should be connected to 328P.

Ceramic Capacitor

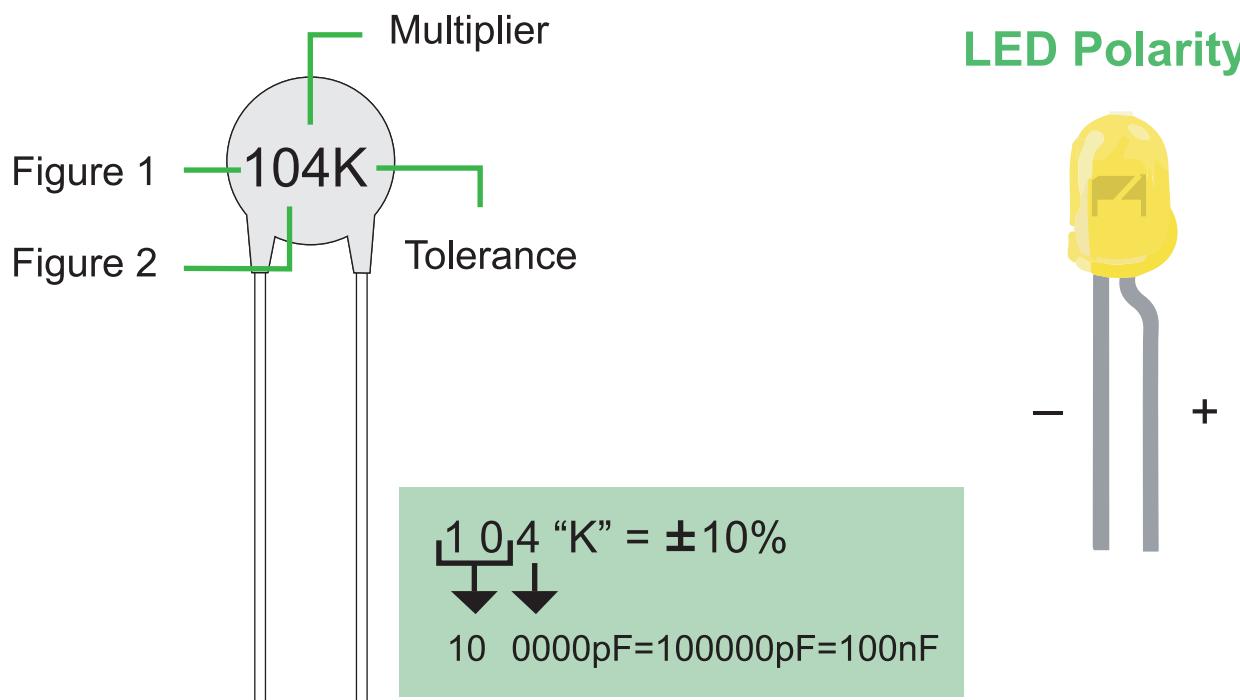

VALUE (F1 & 2)	MULTIPLIER	LETTER	TOLERANCE
0	1	B	$\pm 0.1\text{pF}$
1	10	C	$\pm 0.25\text{pF}$
2	10^2	D	$\pm 0.5\text{pF}$
3	10^3	F	$\pm 1\%$
4	10^4	G	$\pm 2\%$
5	10^5	H	$\pm 3\%$
6	N/A	J	$\pm 5\%$
7	N/A	K	$\pm 10\%$
8	0.01	M	$\pm 20\%$
9	0.1	Z	$\pm 80\%/-20\%$